

Assignment -1
Smart Home using Tinkercad


Assignment Date	09 November 2022
Student Name	Ms. Vijayalakshmi K
Student Roll Number	717819L255
Maximum Marks	2 Marks

Question-1:

Build a smart home in Tinkercad with 2 sensors, an Led, buzzer and submit it.

Solution:

Circuit Diagram:

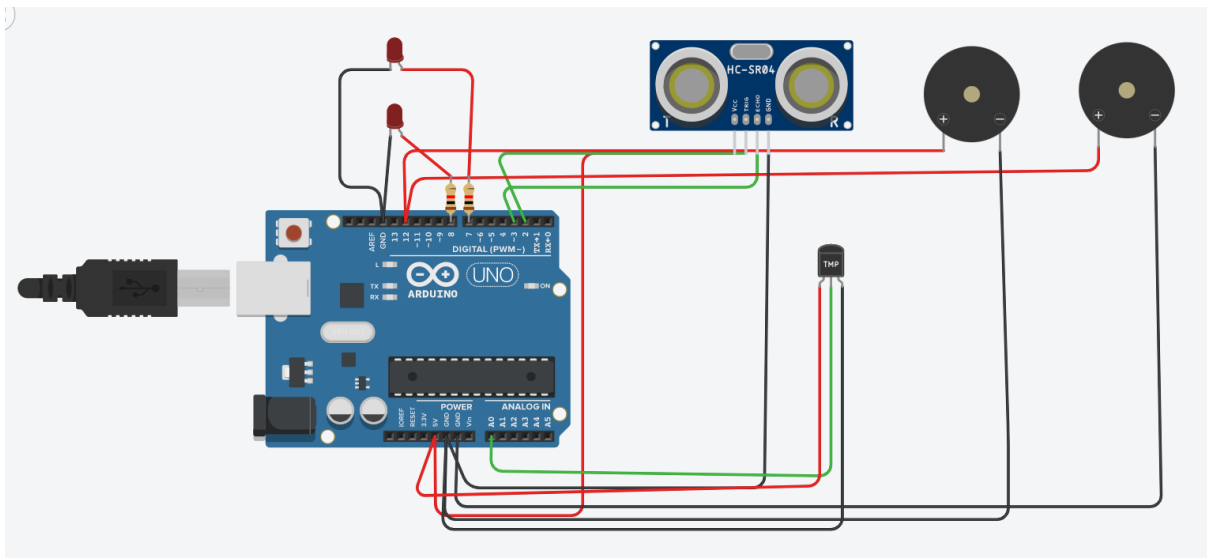

Source Code:

```
int temp=2;
int e=3;
void setup()
{
  Serial.begin(9600);
  pinMode(temp,OUTPUT);
  pinMode(e,INPUT);
  pinMode(12,OUTPUT);
}
void loop()
{
  float dur=pulseIn(e,HIGH);
  float dis=(dur*0.0343)/2;
  Serial.print("Distance is: ");
  Serial.println(dis);
}
```

```

//LED ON
if(dis>=100)

{
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
}
if(dis>=100)
{
for(int i=0; i<=30000; i=i+10)
{
tone(12,i);
delay(1000);
noTone(12);
delay(1000);
}
}
double a=analogRead(A0);
temp=((a/1024)*5)-0.5)*100;
Serial.print("Temp Value: ");
Serial.println(temp);
delay(1000);
if(t>=100)
{
digitalWrite(8,HIGH);
digitalWrite(7,HIGH);
}
if(temp>=100)
{
for(int i=0; i<=30000; i=i+10)
{
tone(12,i);
delay(1000);
noTone(12);
delay(1000);
}
}
if(temp<100)
{

digitalWrite(8,LOW);

digitalWrite(7,LOW);

}

```

}

Simulation Output:

